

Johnson Le


Cmpe167

February 12, 2019

Homework 2

Question 1:

$$(a) C = \frac{\epsilon_r \epsilon_0 \cdot \text{area}}{d} = \frac{(20)(8.854 \times 10^{-12} \text{ F/m})(0.01)}{0.001} = 1.77 \text{ nF}$$

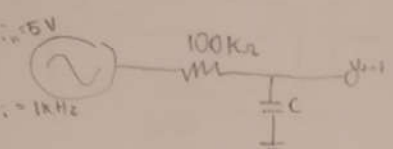(b) 

$$f_c = \frac{1}{2\pi RC} = 899.8 \text{ Hz} \approx 900 \text{ Hz}$$

$$R_c = \frac{1}{2\pi f_c C} = 89.9 \text{ k}\Omega \approx 90 \text{ k}\Omega$$

$$V_{out}(1 \text{ kHz}) = V_{in} \cdot \frac{R_c}{\sqrt{R^2 + R_c^2}} = 3.718 \text{ V}$$

$$(c) X(\omega) = 1 \times 10^{-3} s - 0.004 \omega$$

$$X(0) = 0.001$$

$$X(70 \text{ kHz}) = 1 \times 10^{-3} s - 0.004(70) = -0.279$$

$$C(70 \text{ kHz}) = C \cdot \frac{X(0)}{X(70 \text{ kHz})} = 1.77 \text{ nF} \cdot \frac{0.001}{-0.279} = -6.344 \text{ pF}$$



$$R_c(70 \text{ kHz}) = \frac{1}{2\pi f_c C(70)} = 25.01 \text{ M}\Omega$$

$$V_{out}(1 \text{ kHz}, 70 \text{ kHz}) = 5 \text{ V} \cdot \frac{25 \text{ M}}{\sqrt{100 \text{ k}^2 + 25 \text{ M}^2}} \approx 5 \text{ V}$$

$$\text{range: } [3.718, 5]$$

(d) If burglar is on the mat but not still, as long as one foot is on the mat and the other in air/on mat, it should still be 78 kg

If burglar shuffling on/off the its going to flicker inbetween 3.718 & 5

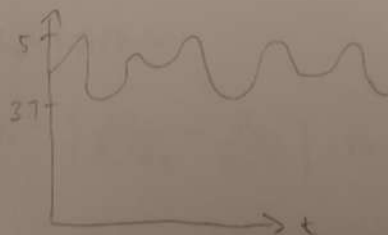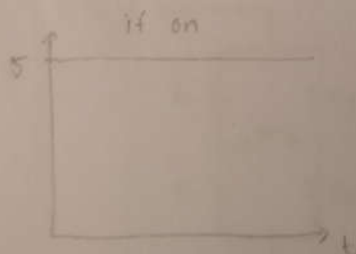

Question 2:


$$N = 10^{-3} \text{ m/s}^2$$

$$R_0 = 1 \text{ k}\Omega$$

$$GF = 3$$

$$E = 73.1 \text{ GPa} = 731000 \text{ N/cm}^2$$

$$R_w = 1 \text{ k}\Omega$$

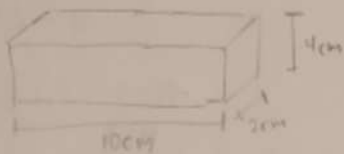

$$L_0 = 10 \text{ cm}$$

$$t = 2 \text{ cm}$$

$$w = 4 \text{ cm}$$

$$\epsilon = \frac{4LF}{Ewt^2}$$

$$GF = \frac{\Delta R/R}{\epsilon}$$

(a)

$$W_L = 1 \text{ kg} \Rightarrow F = 1000 \cdot 9.8 = 9800 \text{ N}$$


$$\epsilon = \frac{4(10 \text{ cm})(9800 \text{ N})}{(7.31 \times 10^4 \text{ N/cm}^2)(4 \text{ cm})(2 \text{ cm})^2} = \frac{4(10)(9800)}{(7.31 \times 10^4 \cdot \frac{1}{\text{cm}^2})(4)(4 \text{ cm}^2)}$$

$$= 3.35 \times 10^{-3}$$

$$GF = \frac{\frac{R_L - R_0}{R_0}}{\epsilon} \Rightarrow GF = \frac{R_L - R_0}{\epsilon \cdot R_0} \Rightarrow R_L = (GF \cdot \epsilon \cdot R_0) + R_0$$

$$R_L = (3)(3.35 \times 10^{-3})(1 \times 10^3 \Omega) + (1 \times 10^3 \Omega) = 1.01 \text{ k}\Omega$$

(b)

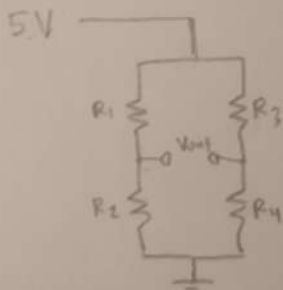

$$\text{assuming } R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

$$R_4 = 1.01 \text{ k}\Omega$$

$$V_o = \left[\frac{R_4}{R_2 + R_4} - \frac{R_3}{R_1 + R_3} \right] \cdot V_{in}$$

Question 3

(a) $f_c = 100 \text{ Hz}$, $\Delta T = 0$

$$\text{Noise} = N$$

$$N_o(@f_c) = 600$$

$$N_n(@f_c) = 600 \cdot 0.707 = 424.2$$

$$N_n(@1 \text{ kHz}) \approx 300$$

(b) $f_c = 1 \text{ Hz}$

$$N_o(f_c) \approx 1200 \quad \text{assuming slope} \approx - \frac{1200 - 800}{10 - 1} = - \frac{400}{9}$$

$$N_n(@f_c) = 848.4$$


Question 4

$$R = (1k\Omega) \left[1 + \frac{F}{200N} \right]$$

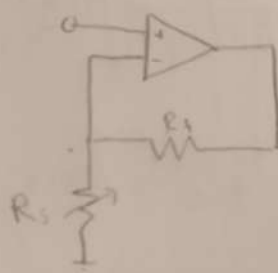(a) $R_o = 1k\Omega$, $R_{so} = 1.25k\Omega$


Going to use $V_{in} = 5V$

Plan is to make a circuit with sensor and get some range of $V_{out1} = V_x$
then map that range using some bias and scaling to V_{out} range 0-4V.
Assuming ideal op-amps and




if R_f is 1000Ω ,
the gain from this amplifier
ranges from $A \Rightarrow [1.8, 2]$

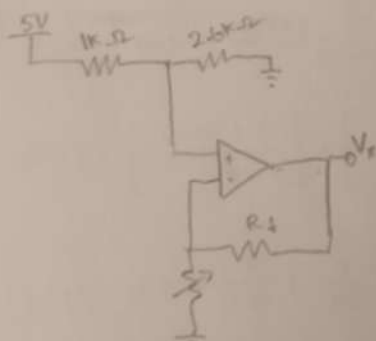gonna input 2V by adding voltage divider to V_{in}




The range of V_x is now $[1.8 \cdot 2, 2 \cdot 2]$
 $= [3.6, 4]$

to create a bias of 3.6V,

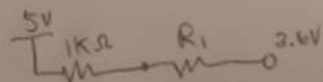

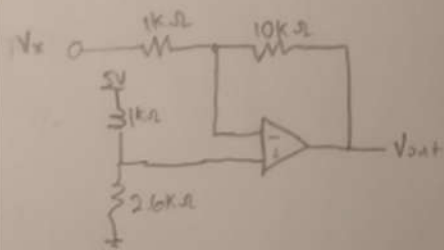I'm going to use only standard resistors
so choosing $R_1 = 2.6k\Omega$ gets roughly 3.6V




Here, if $V_x = 3.6V$, $V_{out} \approx 3.8V$
if $V_x = 4.0V$, $V_{out} = 0V$

if R_1 from earlier was $2.666k\Omega$,
at $V_x 3.6V$, $V_{out} = 4V$

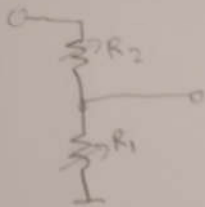Question 5

$$R_1 = 1k\Omega \cdot \left[1 + \frac{F}{1kN} \right], \quad R_2 = 1k\Omega \left[1 - \frac{F}{1kN} \right]$$



Basic voltage divider formula:

$$V_{out} = V_{in} \cdot \frac{R_1}{R_2 + R_1}$$

(a) $V_{out}(F) = V_{in} \cdot R(F)$

$$R(F) = \frac{R_1(F)}{R_2(F) + R_1(F)} = \frac{[1000 + F]}{[1000 - F] + [1000 + F]} = \frac{1000 + F}{2000}$$

$$R(F) = \frac{1000 + F}{2000}$$

$$V_{out}(F) = 5 \cdot R(F) = \frac{1000 + F}{400}$$

(b) $f(x) = f(a) + \frac{f'(a)}{1!}(x-a)^1 + \frac{f''(a)}{2!}(x-a)^2 + \dots$, $x = F$, $a = F_0$

$$f(F) = \left[\frac{1000 + F}{400} \right] + \left[0 + \frac{1}{400} \right] \left[\frac{F - F_0}{2} \right] + 0, \quad F_0 = 0 \text{ in neutral pos}$$

$$f(F) = 2.5 + \frac{F}{400} + \frac{F}{800} = 2.5 + \frac{3F}{800}$$